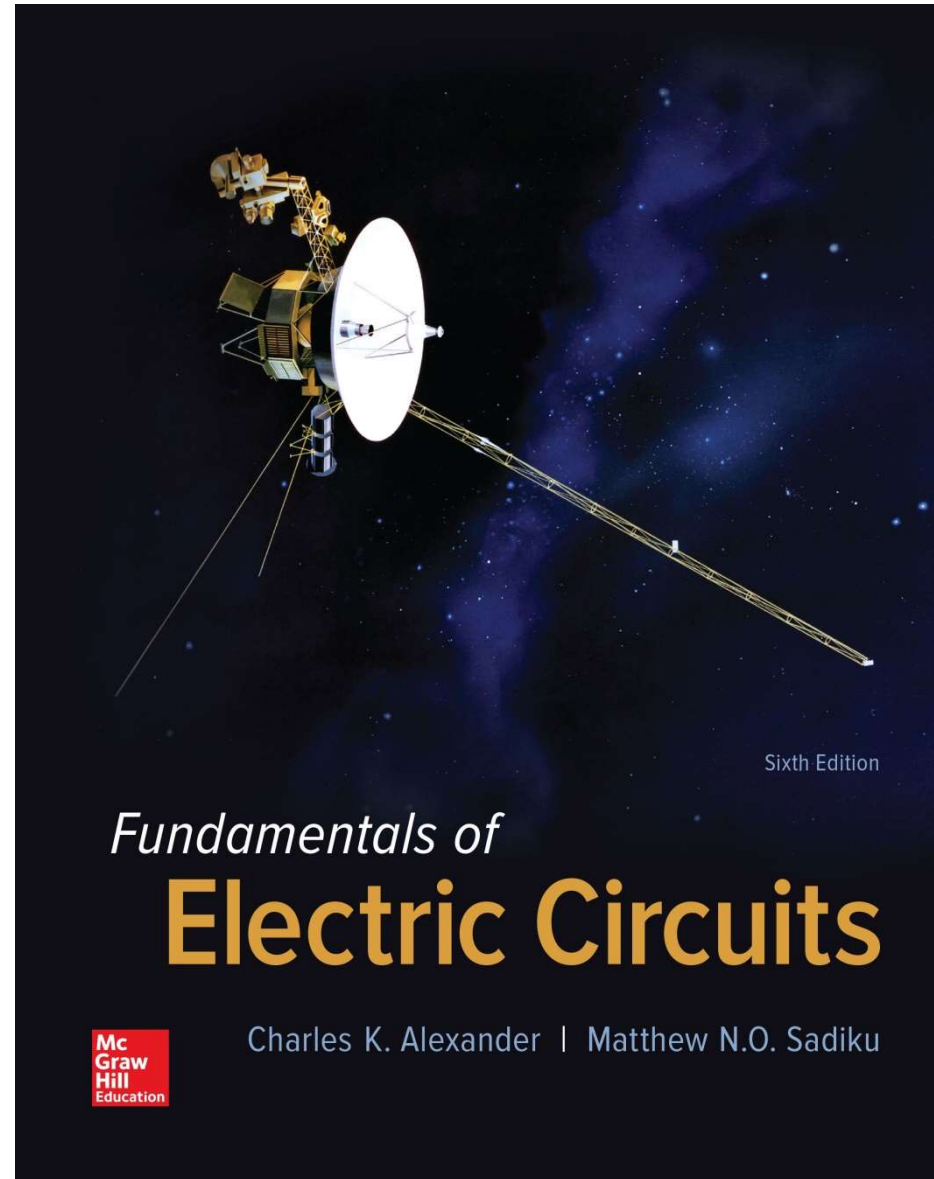


Fundamentals of Electric Circuits Chapter 4



Overview

- **In this chapter, the concept of superposition will be introduced.**
- **Source transformation will also be covered.**
- **Thevenin and Norton's theorems will be covered.**
- **Examples of applications for these concepts will be presented.**

Linearity

- **Linearity in a circuit means that as current is changed, the voltage changes proportionally.**
- **It also requires that the response of a circuit to a sum of sources will be the sum of the individual responses from each source separately.**
- **A resistor satisfies both of these criteria.**

Superposition

- **If there are two or more independent sources there are two ways to solve for the circuit parameters:**
 - Nodal or mesh analysis
 - Use superposition
- **The superposition principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.**

Applying superposition

- Using superposition means applying one independent source at a time
- Dependent sources are left alone
- The steps are:
 1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using the techniques covered in Chapters 2 and 3.
 2. Repeat step 1 for each of the other independent sources.
 3. Find the total contribution by adding algebraically all the contributions due to the independent sources.


Source transformation

- **It is possible to transform a source from one form to another.**
- **This can be useful for simplifying circuits.**
- **The principle behind all of these transformations is equivalence.**

Source transformation II

- A source transformation is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.

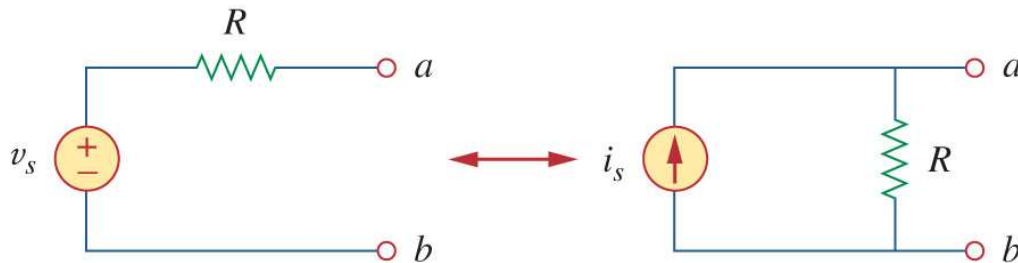Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Terminal equivalency


- These transformations work because the two sources have equivalent behavior at their terminals.
- If the sources are turned off, the resistance at the terminals are both R .
- If the terminals are short circuited, the currents need to be the same.
- From this we get the following requirement:

$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$

Dependent sources

- Source transformation also applies to dependent sources.
- But, the dependent variable must be handled carefully.
- The same relationship between the voltage and current holds here:

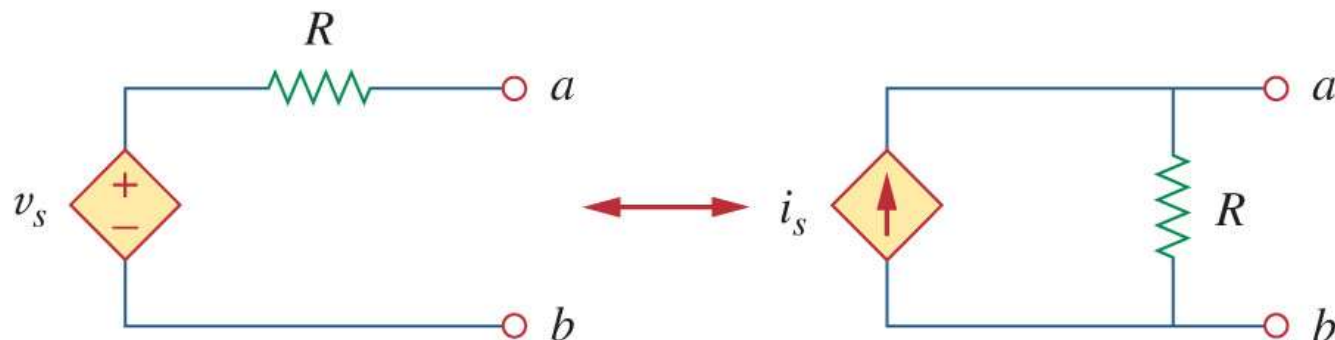Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Source transformation rules

- Note that the arrow of the current source is directed towards the positive terminal of the voltage source.
- Source transformation is not possible when $R=0$ for an ideal voltage source.
- For a realistic source, $R \neq 0$.
- For an ideal current source, $R=\infty$ also prevents the use of source transformation.

(a) Using repeated source transformations, reduce the circuit of Fig. 5.62 to a voltage source in series with a resistor, both of which are in series with the $6\text{ M}\Omega$ resistor. (b) Calculate the power dissipated by the $6\text{ M}\Omega$ resistor using your simplified circuit.

