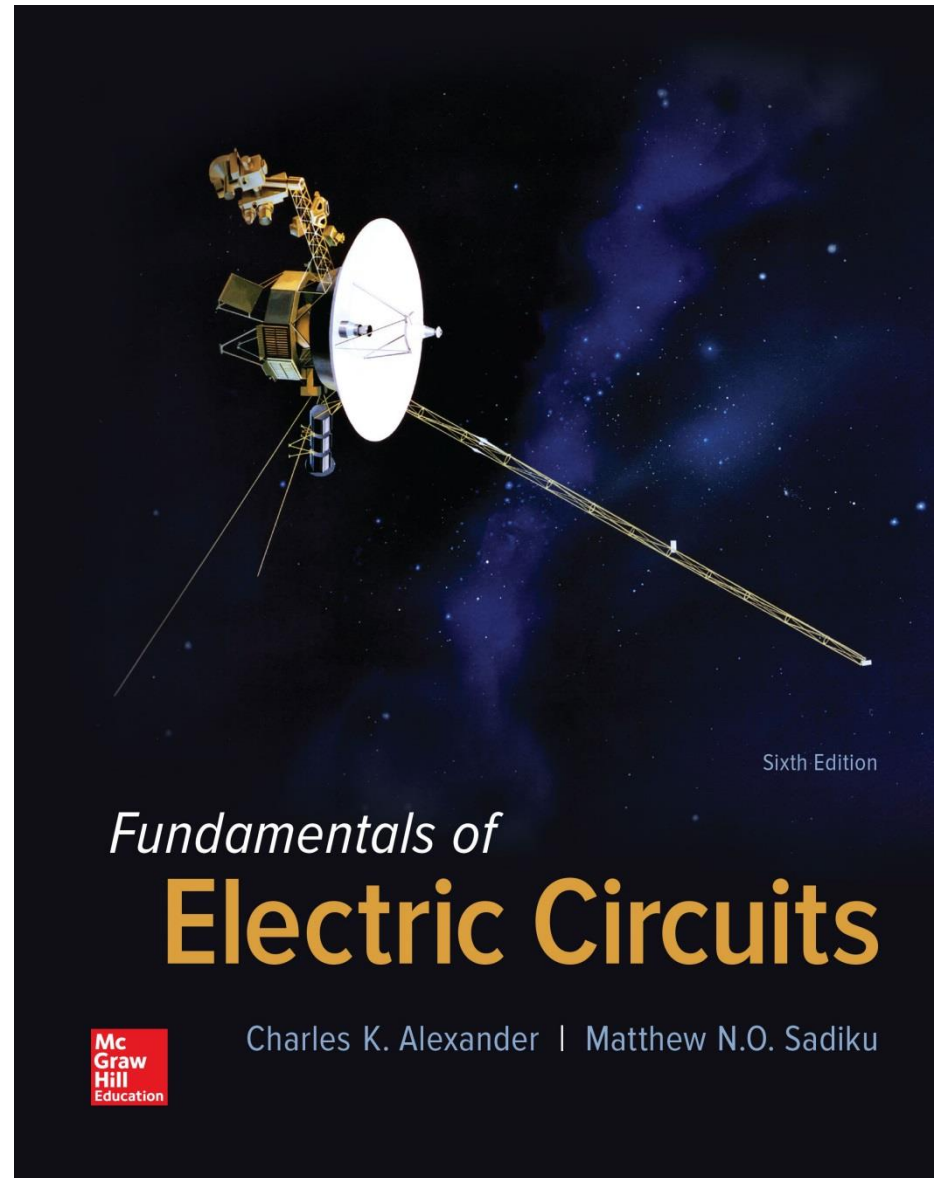


# Fundamentals of Electric Circuits Chapter 5



Copyright © 2017 McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.

# Overview

- **In this chapter, the operation amplifier will be introduced.**
- **The basic function of this useful device will be discussed.**
- **Examples of amplifier circuits that may be constructed from the operation amplifier will be covered.**
- **Instrumentation amplifiers will also be discussed.**



# **Operational Amplifier**

- **Typically called ‘Op Amp’ for short**
- **It acts like a voltage controlled voltage source**
- **In combination with other elements it can be made into other dependent sources**
- **It performs mathematical operations on analog signals**
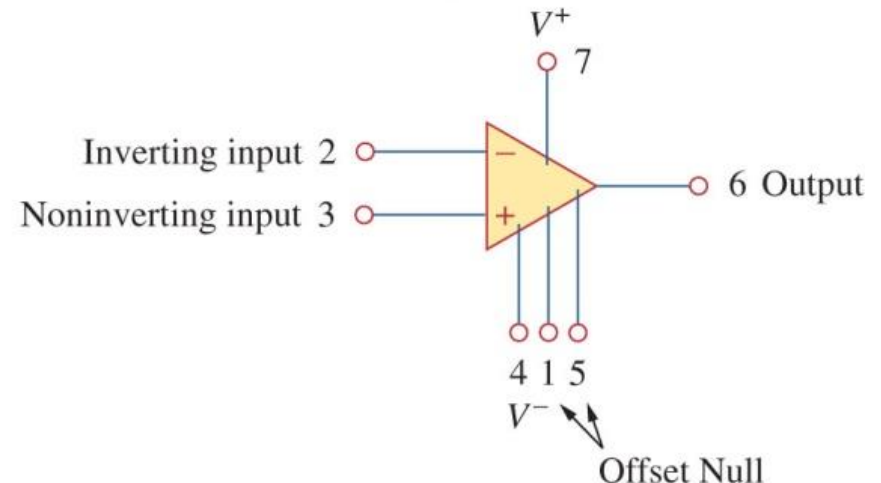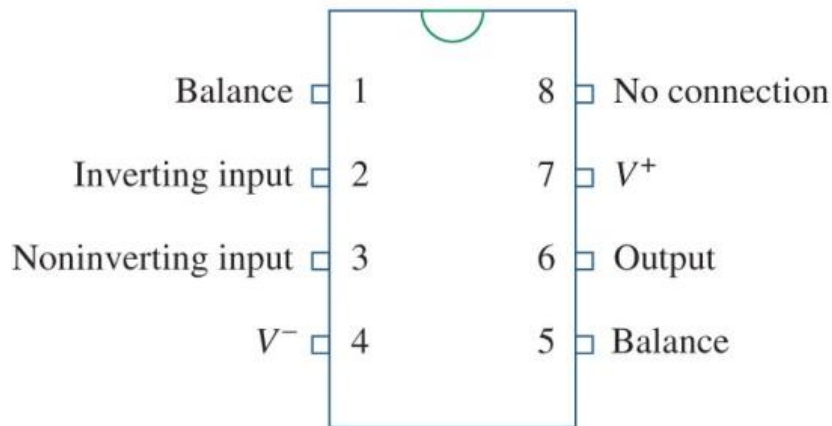
# Operational Amplifier II


- The op amp is capable of many math operations, such as addition, subtraction, multiplication, differentiation, and integration
- There are five terminals found on all op-amps
  - The inverting input
  - The noninverting input
  - The output
  - The positive and negative power supplies

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display


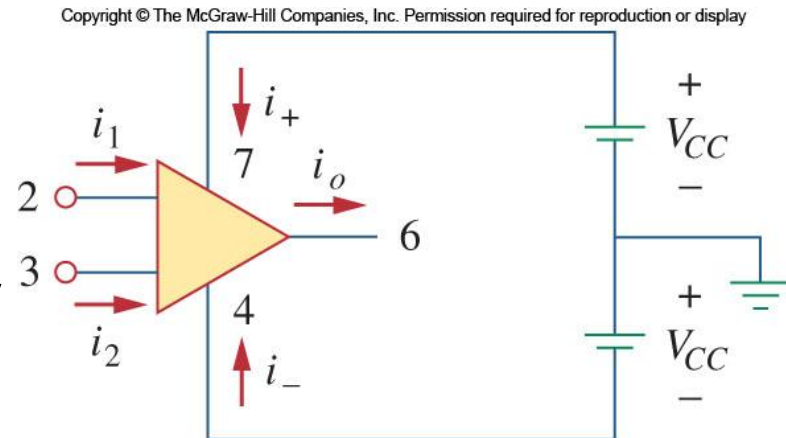
# Powering an Op-amp

- As an active element, the op-amp requires a power source
- Often in circuit diagrams the power supply terminals are obscured
- It is taken for granted that they must be connected
- Most op-amps use two voltage sources, with a ground reference between them
- This gives a positive and negative supply voltage



# Output Voltage

- The voltage output of an op-amp is proportional to the difference between the noninverting and inverting inputs

$$v_o = Av_d = A(v_2 - v_1)$$

- Here,  $A$  is called the open loop gain
- Ideally it is infinite
- In real devices, it is still high:  $10^5$  to  $10^8$  volts/volt

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

**TABLE 5.1**

Typical ranges for op amp parameters.


Parameter	Typical range	Ideal values
Open-loop gain, $A$	$10^5$ to $10^8$	$\infty$
Input resistance, $R_i$	$10^5$ to $10^{13} \Omega$	$\infty \Omega$
Output resistance, $R_o$	10 to $100 \Omega$	$0 \Omega$
Supply voltage, $V_{CC}$	5 to 24 V	

# Feedback

- **Op-amps take on an expanded functional ability with the use of feedback**
- **The idea is that the output of the op-amp is fed back into the inverting terminal**
- **Depending on what elements this signal passes through the gain and behavior of the op-amp changes**
- **Feedback to the inverting terminal is called “negative feedback”**
- **Positive feedback would lead to oscillations**
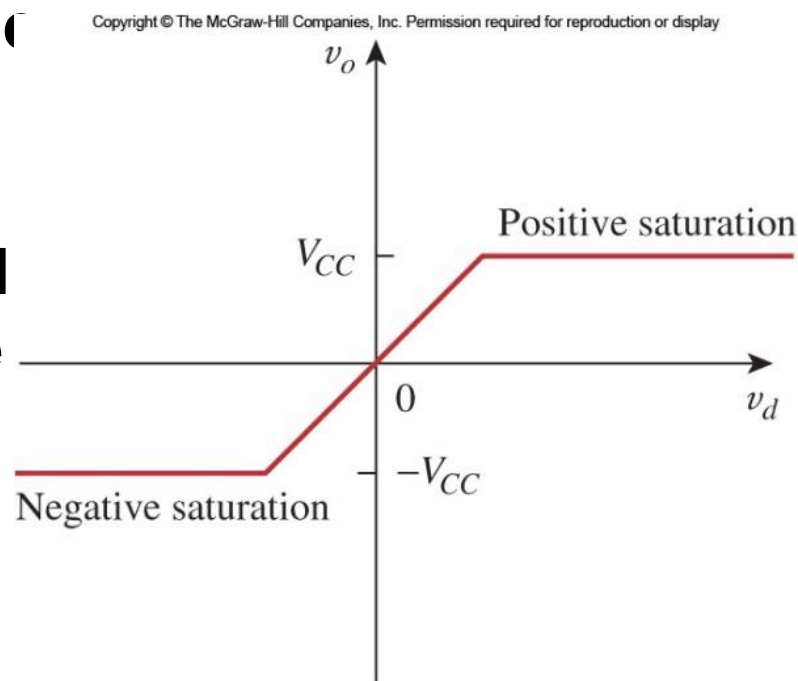
# Voltage Saturation

- As an ideal source, the output voltage would be unlimited
- In reality, one cannot expect the output to exceed the supply voltages
- When an output should exceed the possible voltage range, the output remains at either the maximum or minimum supply voltage
- This is called saturation
- Outputs between these limiting voltages are referred to as the linear region






# **Ideal Op Amp**

- **We give certain attributes to the ideal op-amp**
- **As mentioned before, it will have an infinite open-loop gain**
- **The resistance of the two inputs will also be infinite**
- **This means it will not affect any node it is attached to**
- **It is also given zero output impedance**
- **From Thevenin's theorem one can see that this means it is load independent**
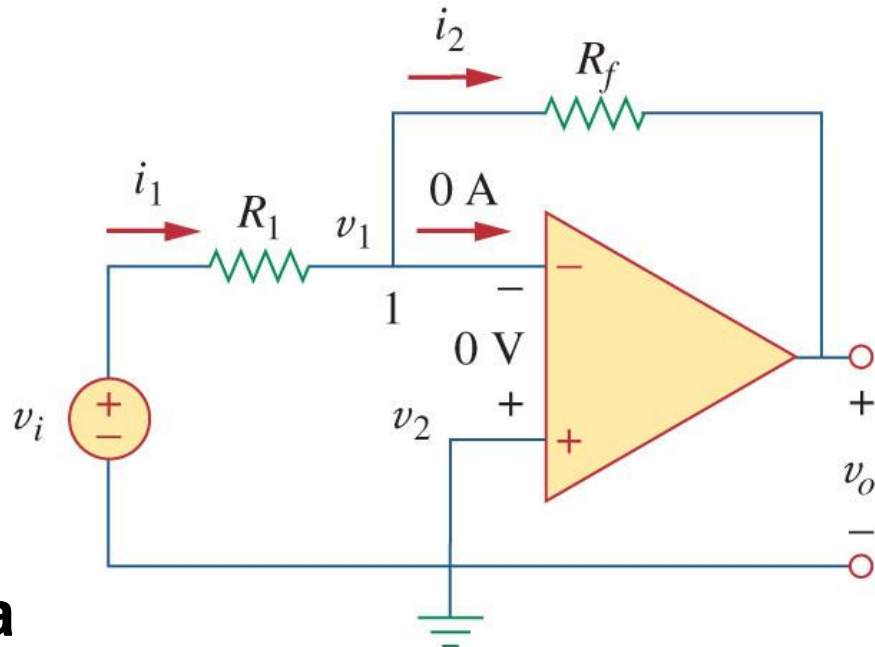
# Inverting Amplifier

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

- The first useful op-amp circuit that we will consider is the inverting amplifier
- Here the noninverting input is grounded
- The inverting terminal is connected to the output via a feedback resistor,  $R_f$
- The input is also connected to the inverting terminal via another resistor,  $R_1$



# Inverting Amplifier III

- This can be rearranged to show the relationship between the input and output voltages


$$v_o = -\frac{R_f}{R_1} v_i$$

- From this one can see that:
  - The gain is the ratio of the feedback resistor and  $R_1$
  - The polarity of the output is the reverse of the input, thus the name “inverting” amplifier
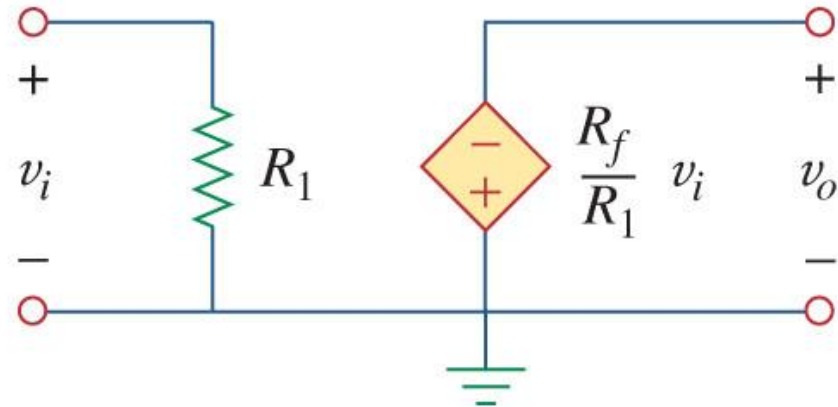
# Equivalent Circuit


- The inverting amplifier's equivalent circuit is shown here
- Note that it has a finite input resistance
- It is also a good candidate for making a current-to-voltage converter

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display


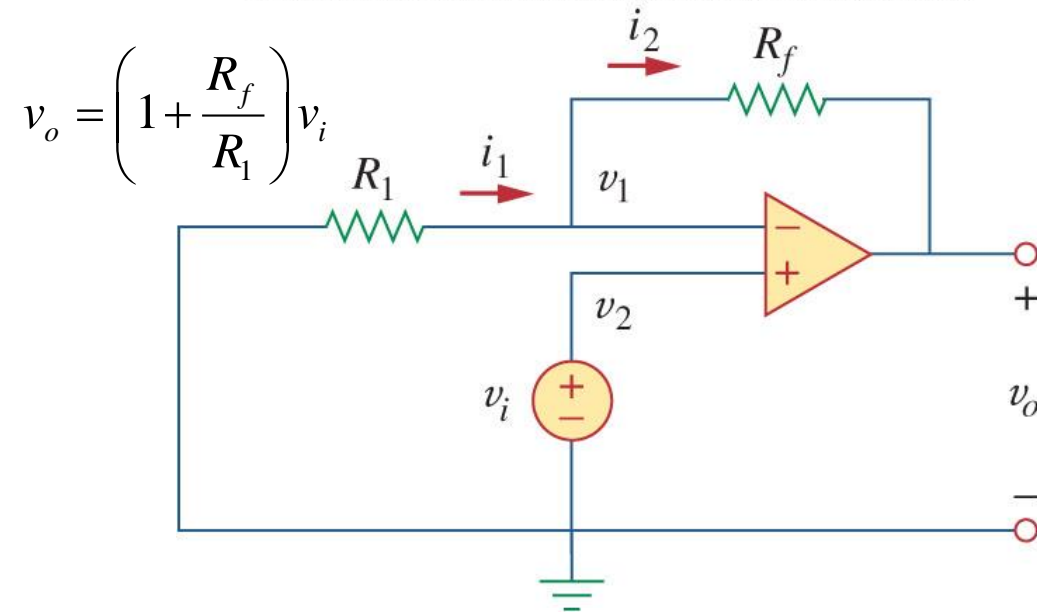
# Non-Inverting Amplifier


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



- Another important op-amp circuit is the noninverting amplifier
- The basic configuration of the amplifier is the same as the inverting amplifier
- Except that the input and the ground are switched

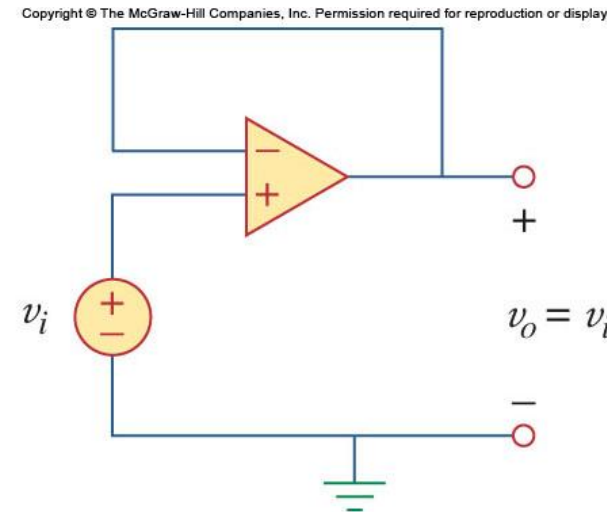
# Non-inverting Amplifier II

- Note that the gain here is positive, thus the amplifier is noninverting
- Also note that this amplifier retains the infinite input impedance of the op-amp
- One aspect of this amplifier's gain is that it can never go below 1.
- One could replace the feedback resistor with a wire and disconnect the ground and the gain would still be 1
- This configuration is called a voltage follower or a unity gain amplifier
- It is good for separating two circuits while allowing a signal to pass through.



# Ejemplo

- Encuentre la ganancia

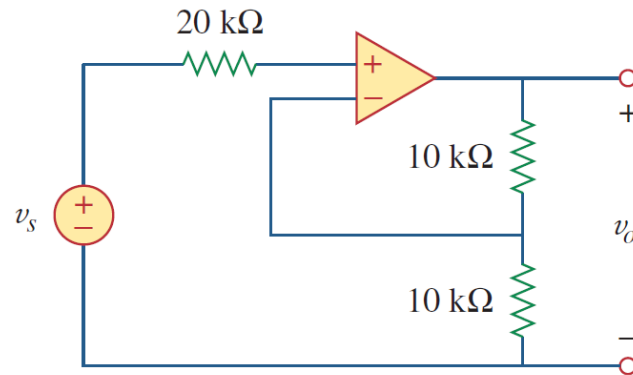






# Ejemplo


- Encuentre  $V_o$  e  $I_o$

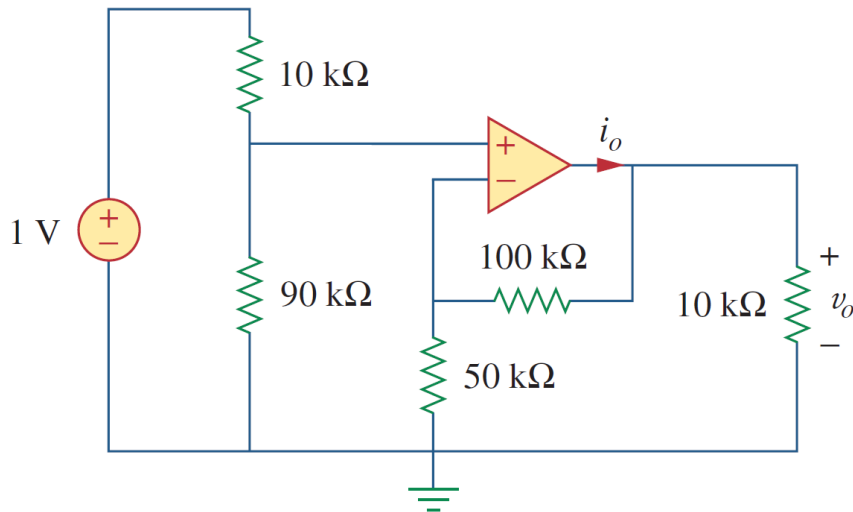



# Ejemplo

- Encontrar  $i_o$

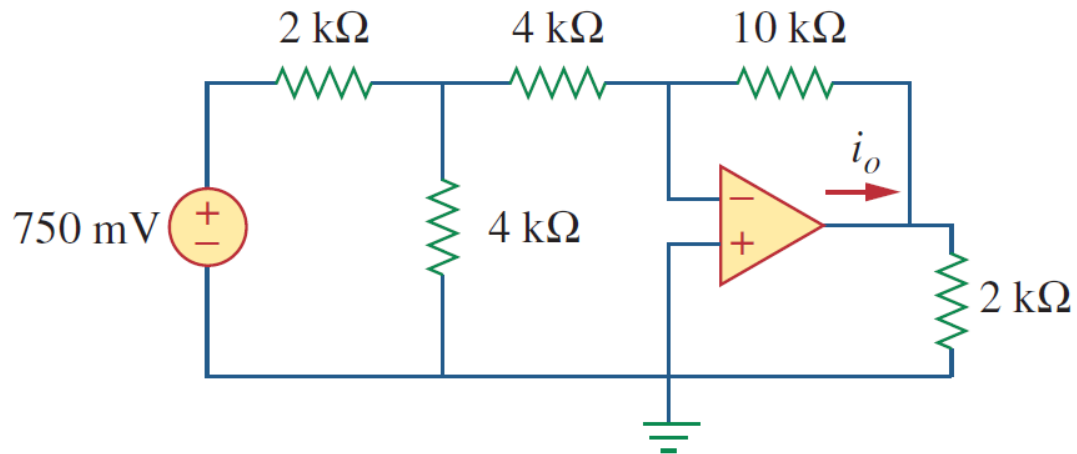



# Ejemplo

- Encontrar  $v_o$  cuando  $v_s = 2\text{ V}$

