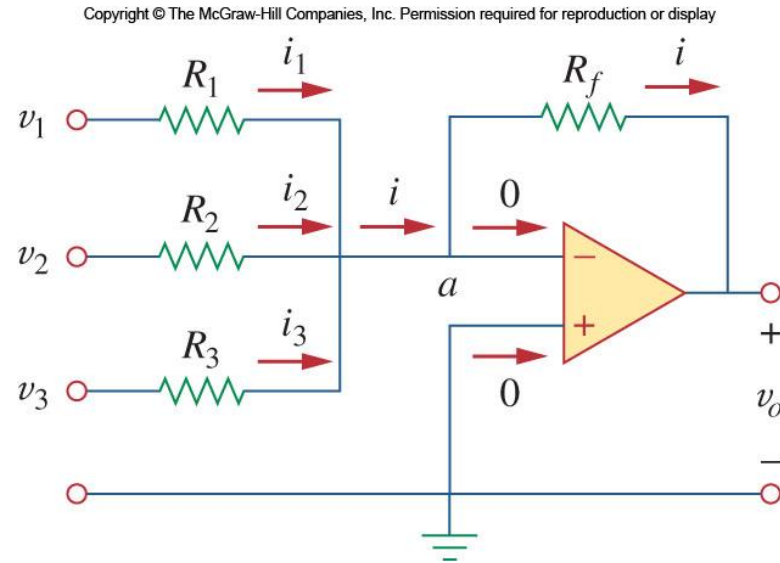


Summing amplifier

- Aside from amplification, the op-amp can be made to do addition very easily.
- If one takes the inverting amplifier and combines several inputs each via its own resistor:
 - The current from each input will be proportional to the applied voltage and the input resistance



$$i_1 = \frac{(v_1 - v_a)}{R_1} \quad i_2 = \frac{(v_2 - v_a)}{R_2} \quad i_3 = \frac{(v_3 - v_a)}{R_3}$$

Summing amplifier II

- At the inverting terminal, these currents will combine to equal the current through the feedback resistor

$$i_a = \frac{(v_a - v_o)}{R_f}$$

- This results in the following relationship:


$$v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$

- Note that the output is a weighted sum of the inputs.
- The number of inputs is not limited to three.

Difference amplifier

- Subtraction should come naturally to the op-amp since its output is proportional to the difference between the two inputs.
- Applying KCL to node a in the circuit shown gives:
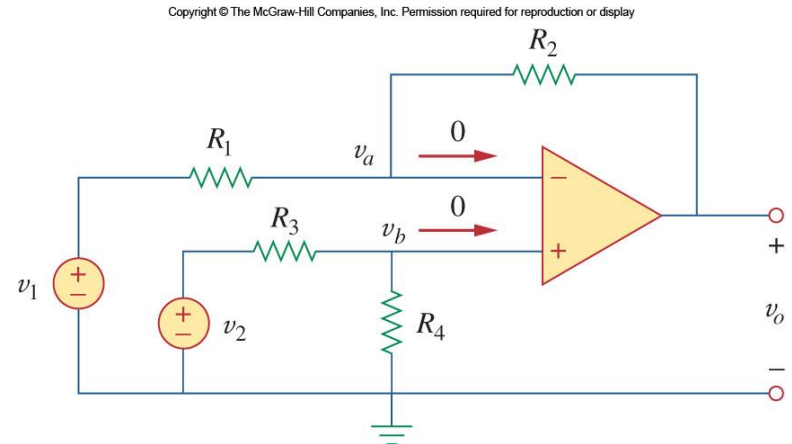
$$v_o = \left(\frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1$$



Difference amplifier II

- Applying KCL to node b gives:

$$v_b = \frac{R_4}{R_3 + R_4} v_2$$

- With the negative feedback present, we know that $v_a = v_b$ resulting in the following relationship:

$$v_o = \frac{R_2 (1 + R_1/R_2)}{R_1 (1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$

Common mode rejection

- It is important that a difference amplifier reject any signal that is common to the two inputs.
- For the given circuit, this is true if:


$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

- At which point, the output is:

$$v_o = \frac{R_2}{R_1}(v_2 - v_1)$$

Cascaded op amps

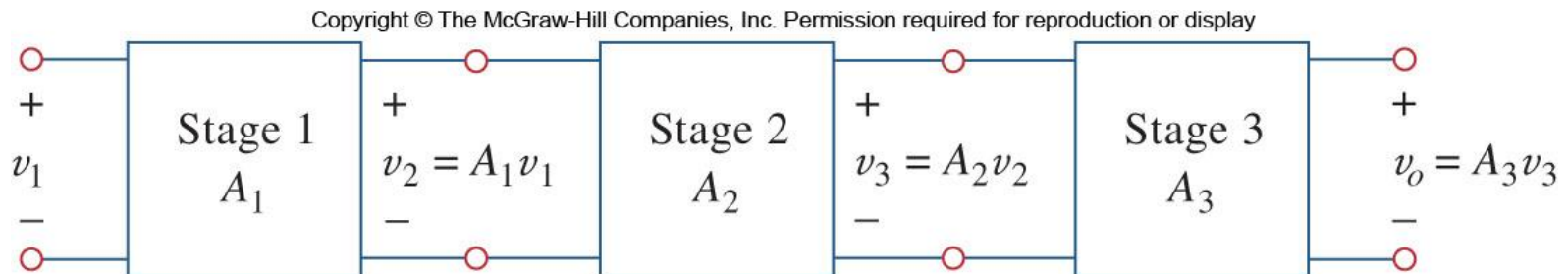- It is common to use multiple op-amp stages chained together.
- This head to tail configuration is called “cascading”
- Each amplifier is then called a “stage”




Cascaded op amps II

- Due to the ideal op-amps' input and output impedance, stages can be chained together without impacting the performance of any one stage.
- One reason for cascading amplifier stages is to increase the overall gain.
- The gain of a series of amplifiers is the product of the individual gains:

$$A = A_1 A_2 A_3$$

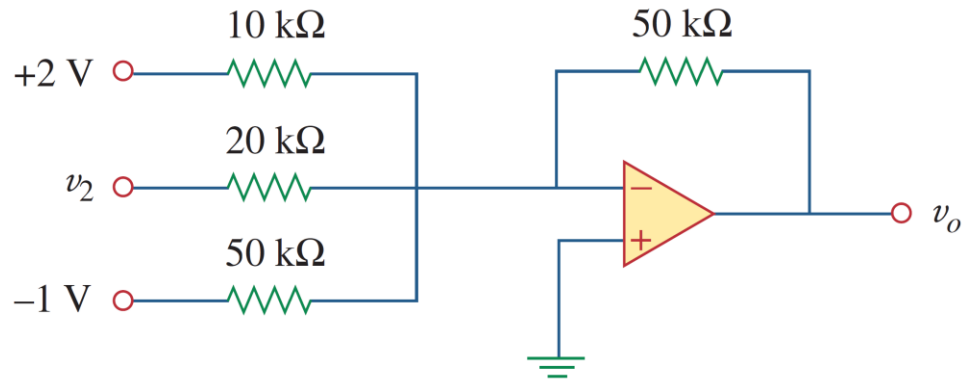5.39 For the op amp circuit in Fig. 5.76, determine the value of v_2 in order to make $v_o = -16.5$ V.



A four-input summing amplifier has $R_1 = R_2 = R_3 = R_4 = 80 \text{ k}\Omega$. What value of feedback resistor is needed to make it an averaging amplifier?

Design an op amp circuit to perform the following operation:

$$v_o = 3v_1 - 2v_2$$

All resistances must be $\leq 100 \text{ k}\Omega$.

