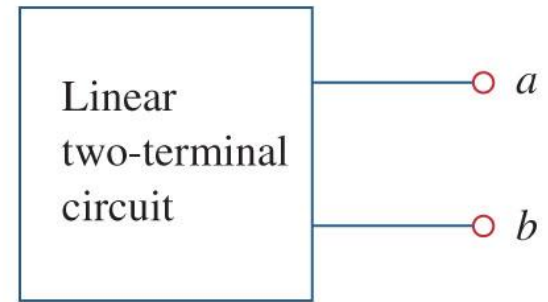



Norton's theorem

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

- Similar to Thevenin's theorem, Norton's theorem states that a linear two terminal circuit may be replaced with an equivalent circuit containing a resistor and a current source.
- The Norton resistance will be exactly the same as the Thevenin.



(a)

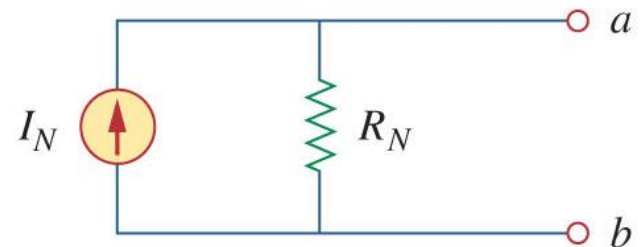


(b)

Norton's theorem II

- The Norton current I_N is found by short circuiting the circuit's terminals and measuring the resulting current.

$$I_N = i_{sc}$$

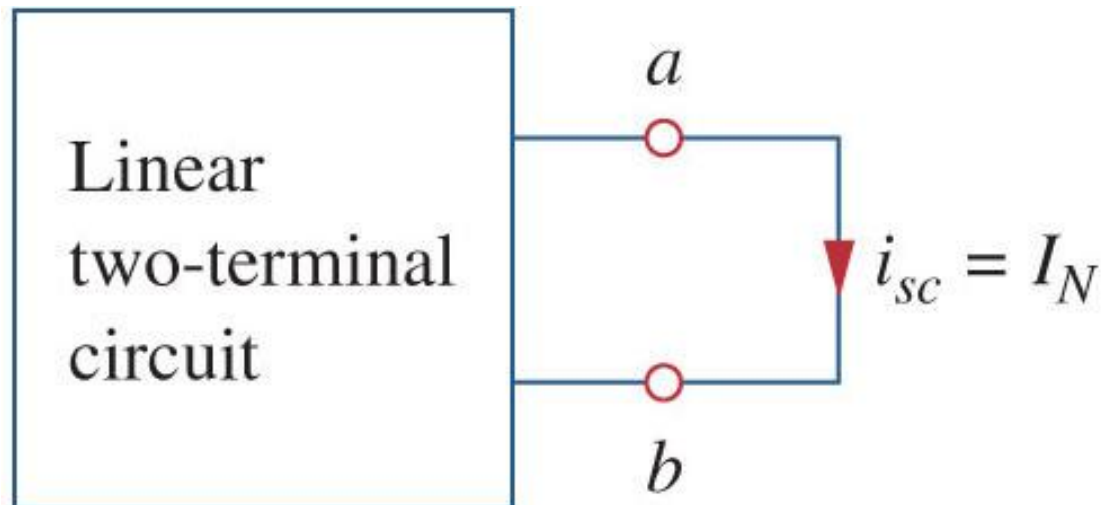


Norton vs. Thevenin


- These two equivalent circuits can be related to each other.
- One need only look at source transformation to understand this.
- The Norton current and Thevenin voltage are related to each other as follows:


$$I_N = \frac{V_{Th}}{R_{Th}}$$

Norton vs. Thevenin II

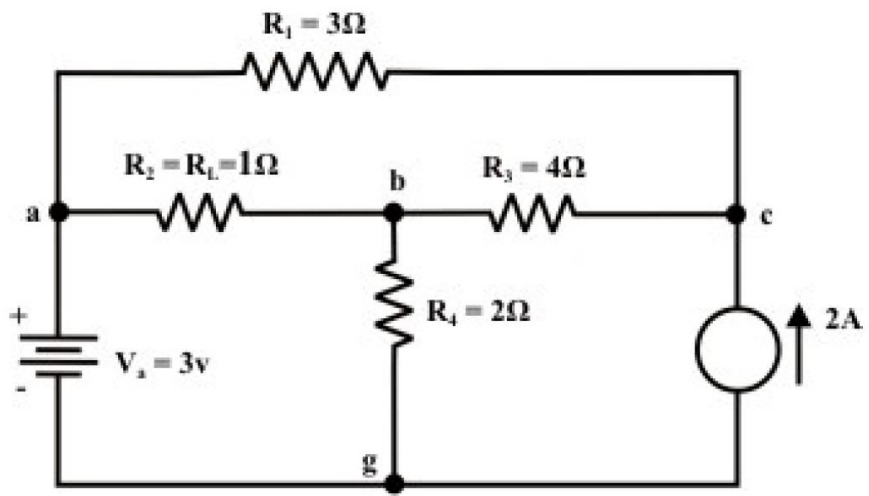- With V_{TH} , I_N , and ($R_{TH}=R_N$) related, finding the Thevenin or Norton equivalent circuit requires that we find:
 - The open-circuit voltage across terminals *a and b*.
 - The short-circuit current at terminals *a and b*.
 - The equivalent or input resistance at terminals *a and b* *when* all independent sources are turned off.



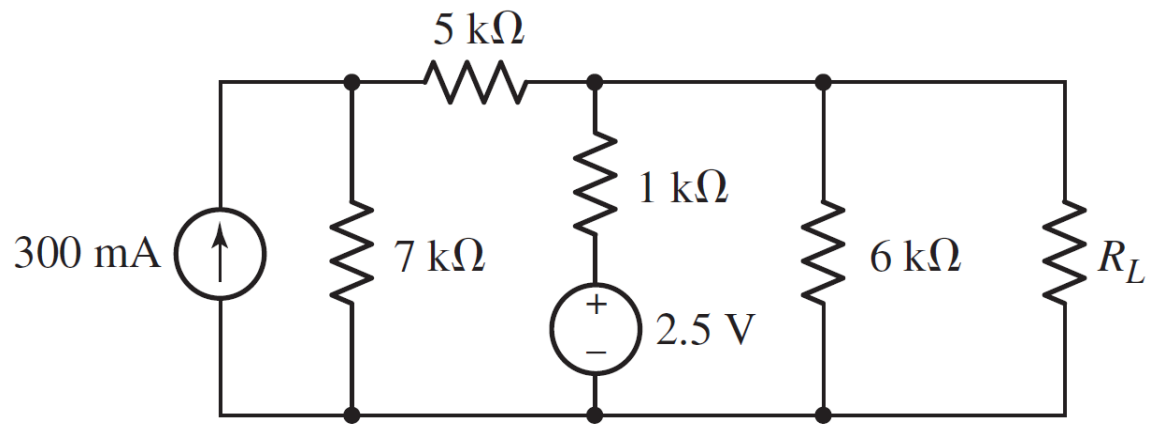

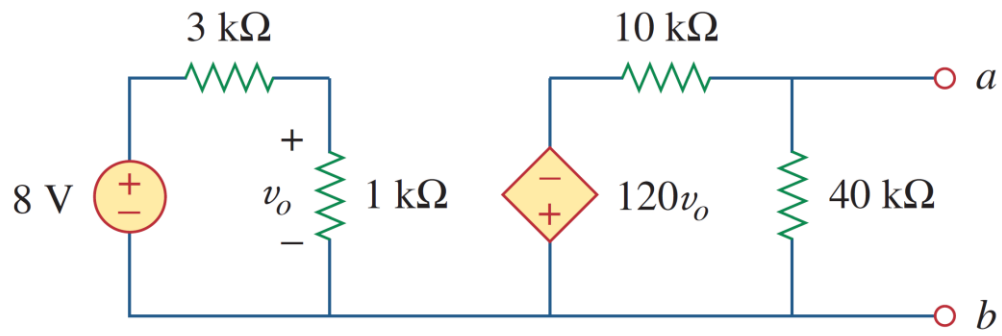

Determinar el valor de R_o para que I_o sea $-10A$.

