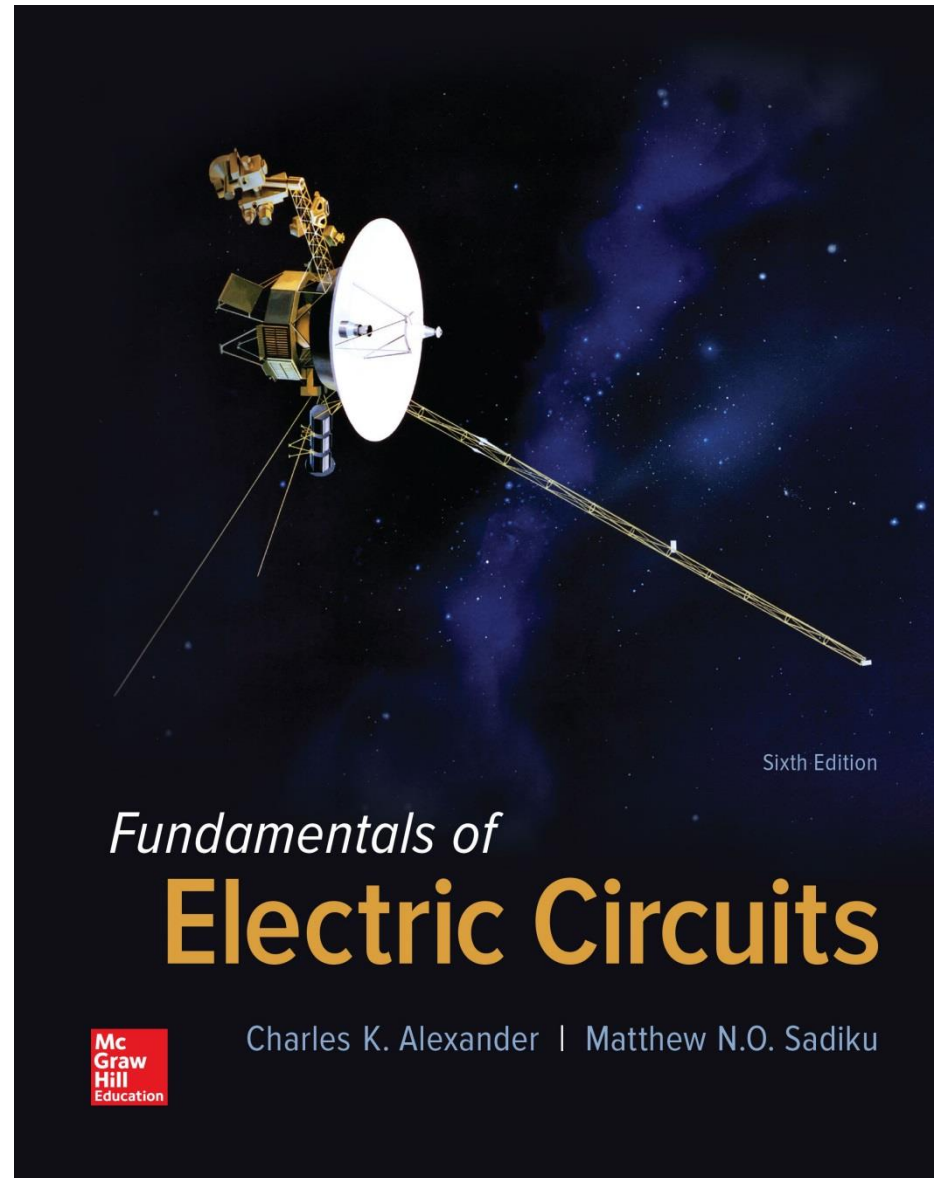


# Fundamentals of Electric Circuits Chapter 4




# **Thevenin's theorem**


- **In many circuits, one element will be variable.**
- **An example of this is mains power; many different appliances may be plugged into the outlet, each presenting a different resistance.**
- **This variable element is called the load.**
- **Ordinarily one would have to reanalyze the circuit for each change in the load.**
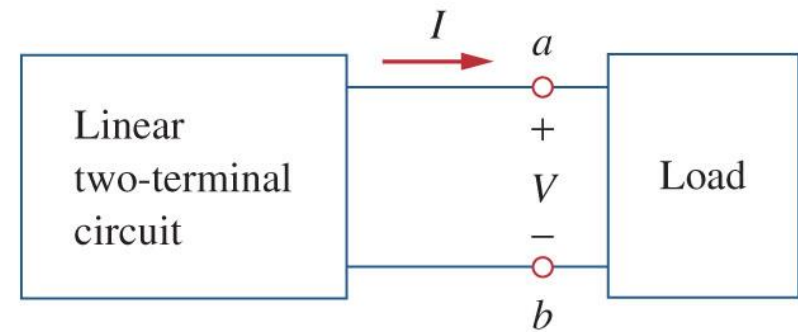
# Thevenin's theorem II

- Thevenin's theorem states that a linear two terminal circuit may be replaced with a voltage source and resistor.
- The voltage source's value is equal to the open circuit voltage at the terminals.
- The resistance is equal to the resistance measured at the terminals when the independent sources are turned off.



(a)

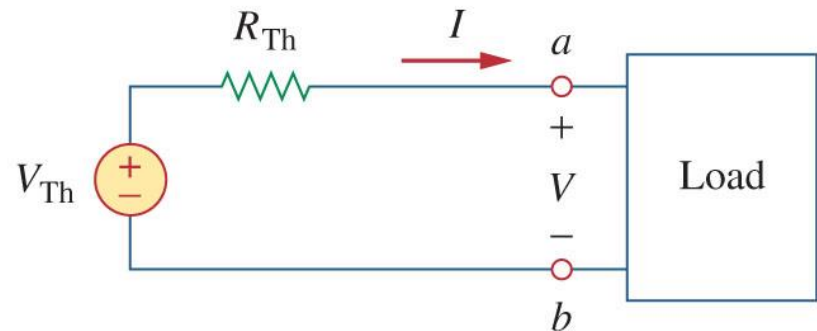


(b)
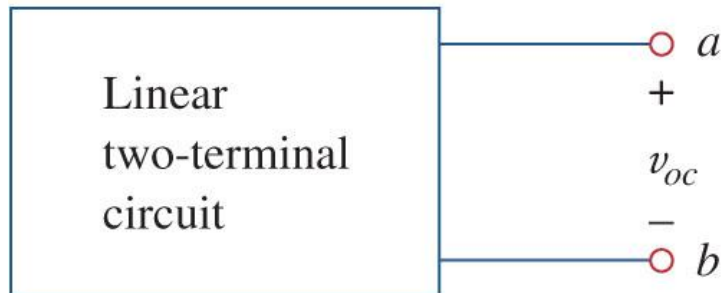
# Thevenin's theorem III


- There are two cases to consider when finding the equivalent resistance.
- **Case 1: If there are no dependent sources, then the resistance may be found by simply turning off all the sources.**

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$V_{Th} = v_{oc}$$

(a)

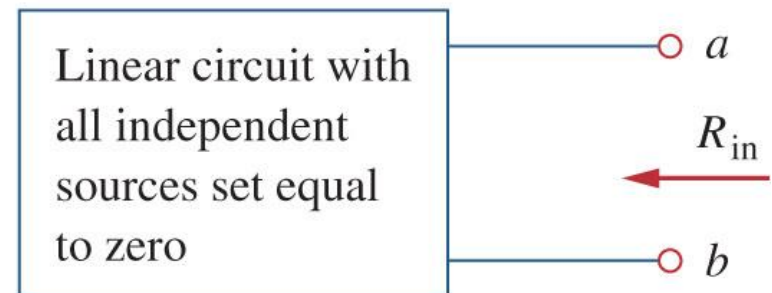


$$R_{Th} = R_{in}$$

(b)

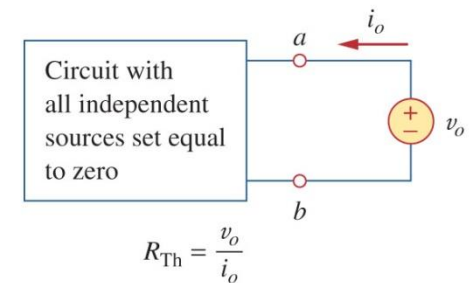
# Thevenin's theorem IV

- **Case 2: If there are dependent sources, we still turn off all the independent sources.**
- **Now apply a voltage  $v_o$  (or current  $i_o$ ) to the terminals and determine the current  $i_o$  (voltage  $v_o$ ).**

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

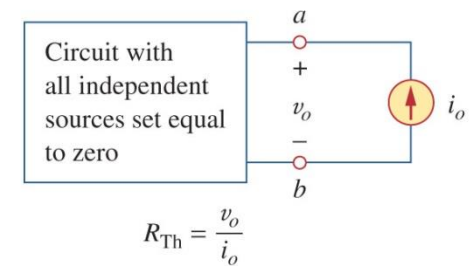

(b)

# Thevenin's theorem V

- Thevenin's theorem is very powerful in circuit analysis.
- It allows one to simplify a circuit
- A large circuit may be replaced by a single independent voltage source and a single resistor.
- The equivalent circuit behaves externally exactly the same as the original circuit.

# Negative resistance?

- It is possible for the result of this analysis to end up with a negative resistance.
- This implies the circuit is supplying power.
- This is reasonable with dependent sources
- Note that in the end, the Thevenin equivalent makes working with variable loads much easier.
- Load current can be calculated with a voltage source and two series resistors.
- Load voltages use the voltage divider rule.

